



**Course Name:** DSD

**Course Number and Section:** 14:332:434:02

**Experiment:** [Experiment # 6 – Spooky registers]

**Lab Instructor:**

**Date Performed:** Today

**Date Submitted:** Tommorrow

**Submitted by:** Kai Gardner – kzg5 : 188002688

**Course Name: DSD**  
**Course Number and Section: 14:332:434:02**

**! Important: Please include this page in your report if the submission is a paper submission. For electronic submission (email or Sakai) please omit this page.**

-----For Lab Instructor Use ONLY-----

GRADE: \_\_\_\_\_

COMMENTS:

--

Electrical and Computer Engineering Department  
School of Engineering  
Rutgers University, Piscataway, NJ 08854  
ECE Lab Report Structure

1. Purpose / Introduction / Overview – describe the problem and provide background information
2. Approach / Method – the approach took, how problems were solved
3. Results – present your data and analysis, experimental results, etc.
4. Conclusion / Summary – what was done and how it was done

This page is unintentionally left blank.

```

module top(
    input logic      clk,
    input logic      rst,
    input logic [1:0] sw, // selects instruction: 1=LW example, 2=SW example
    output logic [31:0] ALUResult, // observable for pre-lab
    output logic [31:0] RD1, RD2, // RF read ports (visible)
    output logic [31:0] probe_register_file, // RF[1] probe
    output logic [31:0] probe_data_memory, // DM[2] probe
    output logic [6:0] display_led // in-lab (seven-seg segments)
);

// I-type instruction examples from the lab handout
// LW: op=010101, rs=00000, rt=00001, imm=...0101 (5)
localparam logic [31:0] INST_LW = 32'b010101_00000_00001_0000_0000_0101;
// SW: op=010100, rs=00000, rt=00110, imm=...0010 (2)
localparam logic [31:0] INST_SW = 32'b010100_00000_00110_0000_0000_0010;

logic [31:0] instr;
logic [7:0] memProdeInd; // DM probe index (0..255)
logic [4:0] regProdeInd; // RF probe index (0..31)
always_comb begin
    // defaults to avoid latches
    instr = 32'b0;
    memProdeInd = 8'd0;
    regProdeInd = 5'd0;
    unique case (sw)
        2'b01: begin
            instr = INST_LW;
            memProdeInd = 8'd5; // observe DM[5]
        end
    endcase
end

```

```

logic [31:0] instr;
logic [7:0] memProdeInd; // DM probe index (0..255)
logic [4:0] regProdeInd; // RF probe index (0..31)
always_comb begin
    // defaults to avoid latches
    instr = 32'b0;
    memProdeInd = 8'd0;
    regProdeInd = 5'd0;
    unique case (sw)
        2'b01: begin
            instr = INST_LW;
            memProdeInd = 8'd5; // observe DM[5]
            regProdeInd = 5'd1; // observe RF[1]
        end
        2'b10: begin
            instr = INST_SW;
            memProdeInd = 8'd2; // observe DM[2]
            regProdeInd = 5'd6; // observe RF[6]
        end
        default: /* NOP */ ;
    endcase
end

// Instruction fields
logic [5:0] op;
logic [4:0] rs, rt, rd;

```

```

// Instruction fields
logic [5:0] op;
logic [4:0] rs, rt, rd;
logic [15:0] imm;
assign op = instr[31:26];
assign rs = instr[25:21];
assign rt = instr[20:16];
assign rd = instr[15:11];
assign imm = instr[15:0];

// Control signals mapped from op: {RegDst, ALUSrc, ALUControl[2:0], MemtoReg}
logic RegDst, ALUSrc;
logic [2:0] ALUControl;
logic MemtoReg;
assign RegDst = op[5];
assign ALUSrc = op[4];
assign ALUControl = op[3:1];
assign MemtoReg = op[0];

// For this lab's two ops: LW (MemtoReg=1) writes reg; SW (MemtoReg=0) writes memory
logic RegWrite, MemWrite;
assign RegWrite = MemtoReg; // LW:1, SW:0
assign MemWrite = ~MemtoReg; // LW:0, SW:1

```

```

// Modules
sign_extend u_se(
    .imm16(imm),
    .signimm(SignImm)
);

mux_regdst u_mux_regdst(
    .RegDst(RegDst), .rt(rt), .rd(rd), .RegDst_out(writeReg)
);

register_file u_rf(
    .clk(clk), .rst(rst), .WE3(RegWrite), .prodeInd(regProdeInd),
    .A1(rs), .A2(rt), .A3(writeReg),
    .WD3(WD3),
    .RD1(RD1), .RD2(RD2),
    .prode(prode_register_file)
);

mux_alusrc u_mux_alusrc(
    .ALUSrc(ALUSrc), .RD2(RD2), .SignImm(SignImm), .ALUSrc_out(srcB)
);

ALU u_alu(
    .SrcA(RD1), .SrcB(srcB), .ALUControl(ALUControl), .ALUResult(ALUResult)
);

```

Data\_memory.sv

```

module data_memory(
    input logic clk, rst,
    input logic [31:0] A,
    input logic [31:0] WD,
    input logic WE,
    input logic [7:0] prodeInd,
    output logic [31:0] RD,
    output logic [31:0] prode
);
    logic [31:0] mem [0:255];

    integer i;
    initial begin
        for (i = 0; i < 256; i = i + 1) begin
            mem[i] = i[31:0];
        end
    end

    assign RD = mem[A[7:0]];

    assign prode = mem[prodeInd];

    always @(posedge clk) begin
        if (WE) begin
            mem[A[7:0]] <= WD;
        end
    end
end
endmodule

```

```
module register_file (  
    input  logic      clk, rst, WE3,  
    input  logic [4:0] A1, A2, A3,  
    input  logic [31:0] WD3,  
    input  logic [4:0] prodeInd,  
    output logic [31:0] RD1, RD2,  
    output logic [31:0] prode  
);  
    logic [31:0] rf [31:0];  
  
    initial begin  
        for (int i = 0; i < 32; i++) rf[i] = i;  
    end  
  
    assign RD1    = rf[A1];  
    assign RD2    = rf[A2];  
  
    assign prode = rf[prodeInd];  
  
    always @(posedge clk) begin  
        if (WE3) rf[A3] <= WD3;  
    end  
endmodule
```



## Muxs

```
module mux_regdst(  
    input logic RegDst, // 0: rt, 1: rd  
    input logic [4:0] rt,  
    input logic [4:0] rd,  
    output logic [4:0] RegDst_out  
);  
    always_comb begin  
        RegDst_out = RegDst ? rd : rt;  
    end  
endmodule
```

```
module mux_memtoereg(  
    input logic MemtoReg, // 0: ALUResult, 1: RD  
    input logic [31:0] ALUResult,  
    input logic [31:0] RD, // from data memory  
    output logic [31:0] MemtoReg_out  
);  
    always_comb begin  
        MemtoReg_out = MemtoReg ? RD : ALUResult;  
    end  
endmodule
```

```
module mux_alusrc(  
    input logic ALUSrc, // 0: RD2, 1: SignImm  
    input logic [31:0] RD2,  
    input logic [31:0] SignImm,  
    output logic [31:0] ALUSrc_out  
);  
    always_comb begin  
        ALUSrc_out = ALUSrc ? SignImm : RD2;  
    end  
endmodule
```

## Sign extender

```

module sign_extend(
    input  logic [15:0] imm16,
    output logic [31:0] signimm
);
    always_comb begin
        signimm = {{16{imm16[15]}}, imm16};
    end
endmodule

```

## Waveform

